

Assignment 1

Ameer Louly

July 2, 2025

Question 1

1)

- The design has 7 inputs and 2 outputs
- Use assign statements to design the following

 


Figure 1: Question

Solution:

```
1  module Q1(A, B, C, D, E, F, sel, out, out_bar);
2
3      input A, B, C, D, E, F, sel;
4      output out, out_bar;
5      wire X1, X2;
6
7      and(X1, A, B, C);
8      xnor(X2, D, E, F);
9      assign out = (sel == 1)? X2 : X1;
10     assign out_bar = ~out;
11
12 endmodule
```

Figure 2: Q1 Code

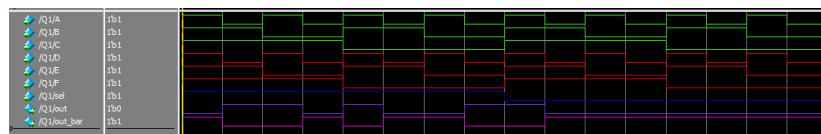


Figure 3: Q1 Waveform

Question 2

- The design has 5 inputs and 2 outputs
 - Inputs
 - i. D -> width = 3
 - ii. A, B, C, Sel -> width = 1
 - Outputs
 - i. Out, out_bar -> width = 1
- Use Behavioral coding style to implement the following

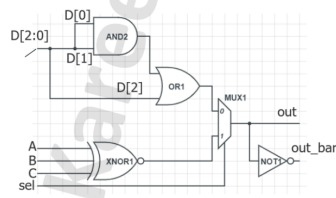


Figure 4: Question

Solution:

```

1  module Q2(D, A, B, C, sel, out, out_bar);
2
3      input [2:0] D;
4      input A, B, C, sel;
5      output out, out_bar;
6      wire AND2, OR1, XNOR1;
7
8      and(AND2, D[0], D[1]);
9      or(OR1, AND2, D[2]);
10     xnor(XNOR1, A, B, C);
11
12     assign out = (sel == 1) ? XNOR1 : OR1;
13     assign out_bar = ~out_bar;
14
15 endmodule

```

Figure 5: Q2 Code

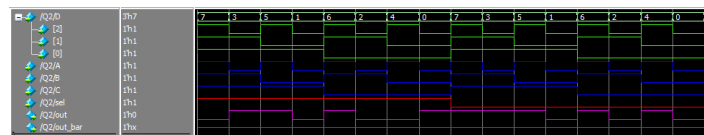


Figure 6: Q2 Waveform

Question 3

Question: Design a 4-bit adder

Solution:

```
1  module Q2(D, A, B, C, sel, out, out_bar);
2
3      input [2:0] D;
4      input A, B, C, sel;
5      output out, out_bar;
6      wire AND2, OR1, XNOR1;
7
8      and(AND2, D[0], D[1]);
9      or(OR1, AND2, D[2]);
10     xnor(XNOR1, A, B, C);
11
12     assign out = (sel == 1) ? XNOR1 : OR1;
13     assign out_bar = ~out_bar;
14
15 endmodule
```

Figure 7: Q3 Code

 


Figure 8: Q3 Waveform

Question 4

4) Implement 2-to-4 Decoder using conditional operator (A logic decoder has n input lines and 2^n output lines. Each output line corresponds to a unique combination of the input values.)

- The design has input A (2 bits) and output D (4 bits)
- you can use the following format for the conditional operator.
- assign <output_signal> = <condition1> ? <value1> : <condition2> ? <value2> : <default_value>;

A ₁	A ₀	D ₃	D ₂	D ₁	D ₀
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Figure 9: Question 4

Solution:

```
1 module Q4_decoder(A, D);
2
3     input [1:0] A;
4     output [3:0] D;
5
6     assign D = (A == 2'b00) ? 4'b0001 :
7                (A == 2'b01) ? 4'b0010 :
8                (A == 2'b10) ? 4'b0100 : 4'b1000;
9
10 endmodule
```

Figure 10: Q4 Code

 


Figure 11: Q4 Waveform

Question 5

Question: Implement an even parity generator module using assign statement.

Solution: Model Generates Even Parity

```
1  module Q5(A, out_with_parity);
2
3      input [7:0] A;
4      output [8:0] out_with_parity;
5
6      assign out_with_parity[8:1] = A;
7      assign out_with_parity[0] = ~^A;
8
9  endmodule
```

Figure 12: Q5 Code

 


Figure 13: Q5 Waveform

Question 6

 


Figure 14: Question 6

Solution:

```

1  module SevenSeg_decoder(A, B, opcode, en, a, b, c, d, e, f, g);
2
3      input [3:0] A, B;
4      input [1:0] opcode;
5      input en;
6      output reg a, b, c, d, e, f, g;
7      wire [3:0] ALU_out;
8
9      ALUx #(4) ALU4bit(A, B, opcode, ALU_out);
10
11     always @(*) begin
12
13         if(en) begin
14             case(ALU_out)
15                 4'd0: {a, b, c, d, e, f, g} = 7'b1111110;
16                 4'd1: {a, b, c, d, e, f, g} = 7'b0110000;
17                 4'd2: {a, b, c, d, e, f, g} = 7'b1101101;
18                 4'd3: {a, b, c, d, e, f, g} = 7'b1111001;
19                 4'd4: {a, b, c, d, e, f, g} = 7'b0110011;
20                 4'd5: {a, b, c, d, e, f, g} = 7'b1011011;
21                 4'd6: {a, b, c, d, e, f, g} = 7'b1011111;
22                 4'd7: {a, b, c, d, e, f, g} = 7'b1110000;
23                 4'd8: {a, b, c, d, e, f, g} = 7'b1111111;
24                 4'd9: {a, b, c, d, e, f, g} = 7'b1111011;
25                 4'd10: {a, b, c, d, e, f, g} = 7'b1110111;
26                 4'd11: {a, b, c, d, e, f, g} = 7'b0011111;
27                 4'd12: {a, b, c, d, e, f, g} = 7'b1001110;
28                 4'd13: {a, b, c, d, e, f, g} = 7'b0111101;
29                 4'd14: {a, b, c, d, e, f, g} = 7'b1001111;
30                 4'd15: {a, b, c, d, e, f, g} = 7'b1000111;
31                 default:
32                     {a, b, c, d, e, f, g} = 7'b0000000;
33             endcase
34         end // End of If statement
35     else
36         {a, b, c, d, e, f, g} = 7'b0000000;
37     end // End of Always block
38
39 endmodule

```

Figure 15: Q6 Code

 


Figure 16: Q6 Waveform